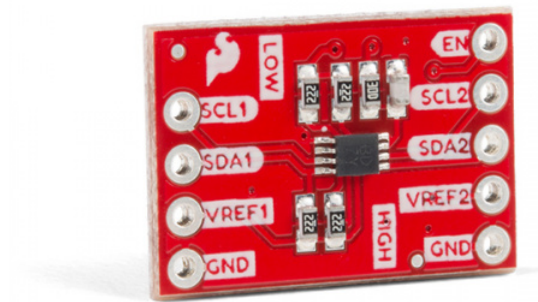


PCA9306 Logic Level Translator Hookup Guide (v2)

Introduction

Heads up! This is for the PCA9306 breakout v2. If you are using the previous PCA9306, you'll want to head over to the older tutorial. The package used on the PCA9306 breakout v2 is different from the PCA9306 breakout v1.

The PCA9306 is a dual bi-directional voltage translator for the I²C-bus and SMBus. It works at a range of voltages between 1.0 and 5.0V and doesn't require a direction pin to function. This is a great board for shifting voltages between sensors and your microcontroller.



SparkFun Level Translator Breakout - PCA9306

● BOB-15439

Product Showcase: SparkFun Level Translator Breakout



Required Materials

To follow along with this tutorial, you will need the following materials. You may not need everything though depending on what you have. Add it to your cart, read through the guide, and adjust the cart as necessary.



Arduino Uno - R3

● DEV-11021



Break Away Headers - Straight

● PRT-00116




USB Cable A to B - 6 Foot

● CAB-00512



SparkFun Triple Axis Accelerometer Breakout - MMA8452Q

● SEN-12756

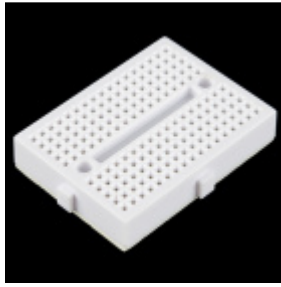

Breadboard - Mini Modular (White)

● PRT-12043



Jumper Wires Premium 4" M/M - 26 AWG (30 Pack)

● PRT-14284

Tools

You will need a soldering iron, solder, and general soldering accessories.



Soldering Iron - 60W (Adjustable Temperature)

● TOL-14456




Solder Lead Free - 15-gram Tube

● TOL-09163


Suggested Reading

 These level converters are pretty easy to start using, but you may want to check out some of the additional reading material below if you are unfamiliar with logic level shifting or haven't worked with Arduino boards prior to this.



How to Solder: Through-Hole Soldering


 
This tutorial covers everything you need to know about through-hole soldering.



What is an Arduino?

What is this 'Arduino' thing anyway?



  

Logic Levels

Learn the difference between 3.3V and 5V devices and logic levels.


I2C

An introduction to I2C, one of the main embedded communications protocols in use today.


Hardware Overview

Power and I²C Sides

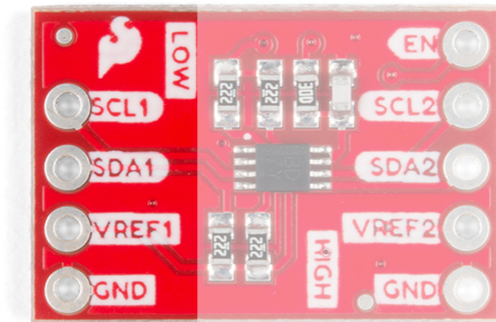At a minimum, the breakout board has seven pins that need to be connected to function properly. VREF1, SCL1, and SDA1 all connect to your lower voltage side.



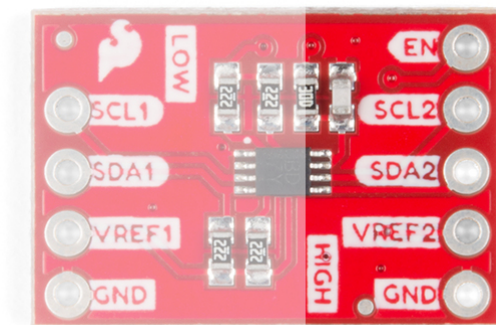VREF2, SCL2, and SDA2 connect to your higher voltage side. One of the GND pins on either side needs to be connected to ground in your system.



What's that extra through-hole on the board labeled as EN? Well, it can be connected to an I/O pin to toggle the PCA9306 from the high side. You'll need to adjust the jumper in the back to be able to use this feature. Check below for more information.


Allowable Voltage Level Translation

For most of the products listed in the catalog, usually you will be translating voltages between **3.3V** and **5V**. However, the datasheet for the PCA9306 states that it can be used to translate lower voltages if you need. Below are the acceptable voltages on the low and high sides.

VREF1 (i.e. Low Side)	VREF2 (i.e. High Side)
1.2V	1.8, 2.5V, 3.3V, 5V
1.8V	2.5V, 3.3V, 5V
2.5V	3.3V, 5V
3.3V	5V

Jumpers

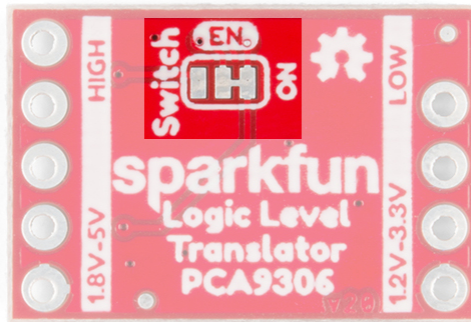There is a jumpers on the underside of this board to turn on and off the PCA9306. By cutting the trace and adding a solder jumper toward the pad labeled as "Switch," you can toggle the logic level translator with your microcontroller.



Enable Feature

It's possible to use the PCA9306 as an I²C *switch*. First, as mentioned above, you'll want to cut the `ON` trace and solder the `Switch` trace. To use the feature you'll attach the high side `VREF2` to you're high side voltage as you normally would, and then attach the `EN` (enable) pin, to a digital Pin. Now when you want to enable I²C communication, pull the line **HIGH**.

Hardware Assembly

To connect the board, you will need to solder headers into the through-holes, and use jumper wires to connect between devices when prototyping. Make sure to place it on a breadboard before soldering to test. You will need to make sure that the headers on each side of the PCA9306 breakout board are soldered at an angle in order for it to sit securely on a breadboard. The board shown at the top of the image shows how the pins are offset and soldered at a small angle. The board shown at the bottom of the image shows pins flush with the board. You will want to make sure that you soldered the pins like the board shown at the top of the image.



Heads up! If you have issues with the bread not sitting flush with the breadboard, try reworking the board adding a blob of solder on the pins and carefully pushing the header outward on a solder mat. After angling the pins, make sure to remove the solder blob on the board and clean the solder joints.


You could also just solder some hookup wire or add a protoshield to connect all of your boards together securely for a project.

Hardware Hookup

For this example, we are going to use an Arduino Uno to connect to an MMA8452 accelerometer breakout board, which runs at 3.3V and communicates over I²C.


3.3V Device (i.e. MMA8452)	PCA9306 (Low Side)	PCA9306 (High Side)	5V Device (i.e. Arduino Uno w/ ATmega328P)
3.3V	VREF1		3.3V
		VREF2	5V
SCL	SCL1	SCL2	A5
SDA	SDA1	SDA2	A4
GND	GND	GND	GND
		EN	Any I/O Pin If Jumper is Adjusted

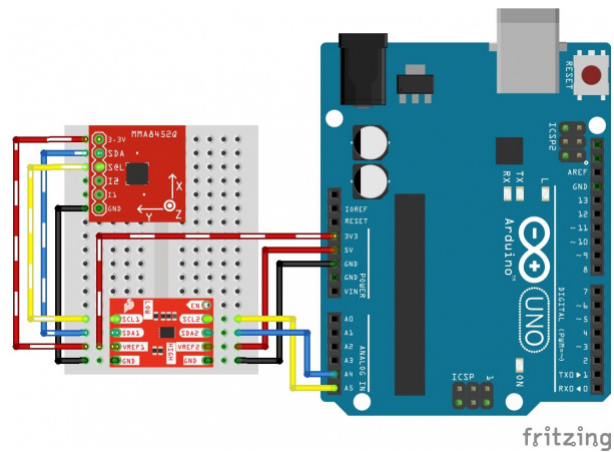Here is a Fritzing diagram showing the actual connections between the MMA8452, the PCA9306 breakout and the Arduino Uno.



You'll need to connect power for the Arduino via the barrel jack, VIN, or USB connector. In this case, we'll simply use power from the USB cable to provide 5V to the high side. The diagram shows the MMA8452 running off the Arduino Uno's 3.3V rail. Keep in mind your power supplies could be different, but you will still need to have a power supply for the lower voltage side of the system and a separate supply for the higher voltage side.

 Once you have the boards physically connected, you are good to go! You don't need to use any special code with the PCA9306 board, and you can simply use any example sketch available for your sensors. In this case, we are using the example MMA8452 from the hookup guide. Head over to the tutorial to finishing programming your Arduino to start using the accelerometer!



MMA8452Q Accelerometer Breakout Hookup Guide

JUNE 11, 2014

How to get started using the MMA8452Q 3-axis accelerometer -- a solid, digital, easy-to-use acceleration sensor.

Resources and Going Further

Now that you know how to use the logic level shifter, it's time to go and use this in your own project! Check out the additional resources below if you have any questions, or leave us feedback on the tutorial itself. Best of luck interfacing with all of your sensors!

- [Schematic \(PDF\)](#)
- [Eagle Files \(ZIP\)](#)

- Datasheet (PDF)
- GitHub Repository
- SFE Product Showcase

Looking to shift the logic levels for a different sensor with the Arduino? Try modifying a Qwiic cable before shifting the logic levels of your I²C device for a Qwiic enabled product.



Qwiic Cable - 50mm

🕒 PRT-14426



SparkFun LTE CAT M1/NB-IoT Shield - SARA-R4

🕒 CEL-14997



Qwiic Expansion Board for Onion Omega

🕒 DEV-15080



SparkFun Qwiic 12 Bit ADC - 4 Channel (ADS1015)

🕒 DEV-15334